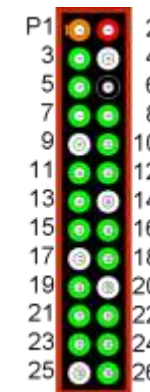


FINDING THE GPIO CONNECTOR PINS 1


Using the Raspberry Pi GPIO connector pins

General Purpose Input Output

Dr James Dalley
dl@richardhale.co.uk



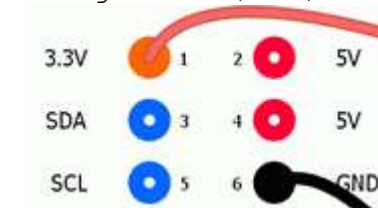1. Find the GPIO pins.
2. Look for the white P1 label for pin 1 (3.3V).
3. Find pin 6 which is ground (GND).




GPIOFlashcardsDLv3.doc

TESTING THAT THE LED WORKS!

2

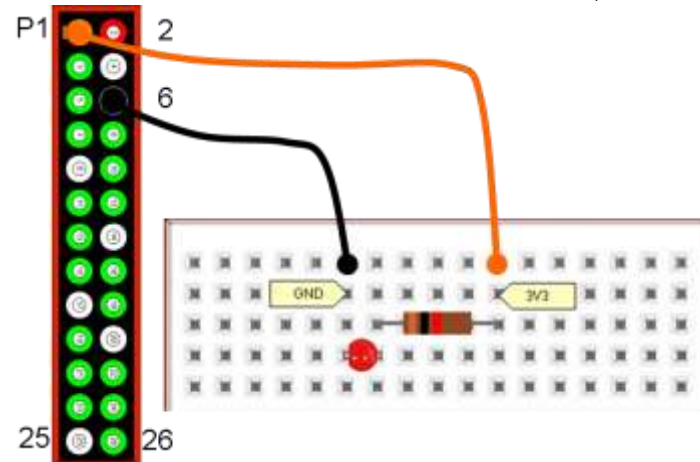Make this circuit (ensure the LED flat spot is on the same side as the GND lead).





GPIOFlashcardsDLv3.doc

GPIOFlashcardsDLv3.doc

BREADBOARD CONNECTIONS & LED 3

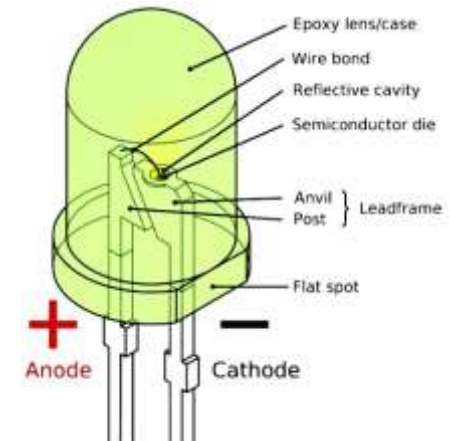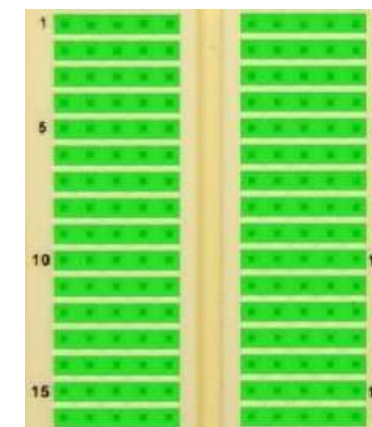Holes in the same coloured bar are connected.



LED: + side has long lead,
- side has short lead and flat spot.

GPIOFlashcardsDLv3.doc

REVISION 1 RASPBERRY PI

4



<http://www.raspberrypi-spy.co.uk/2012/09/raspberry-pi-board-revisions/>

REVISION 2 RASPBERRY PI

6




<http://www.raspberrypi-spy.co.uk/2012/09/raspberry-pi-board-revisions/>

REVISION 1 GPIO CONNECTOR MAP

5

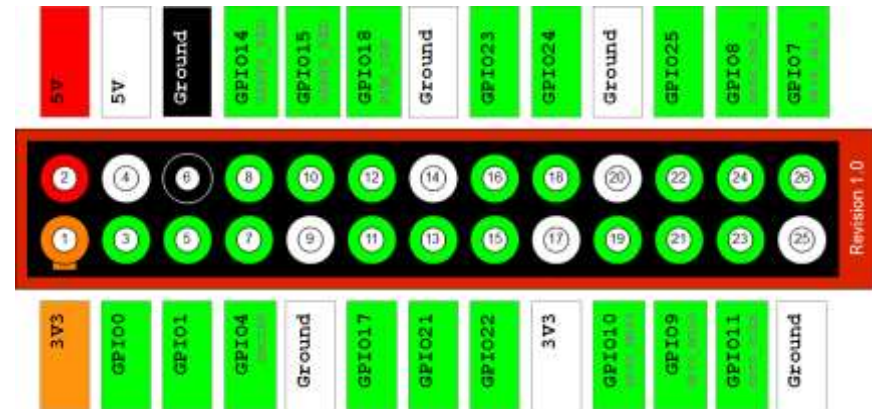The GPIO connector pin numbers are shown within the black box:




<http://www.raspberrypi-spy.co.uk/2012/09/raspberry-pi-board-revisions/>

REVISION 2 GPIO CONNECTOR MAP

7

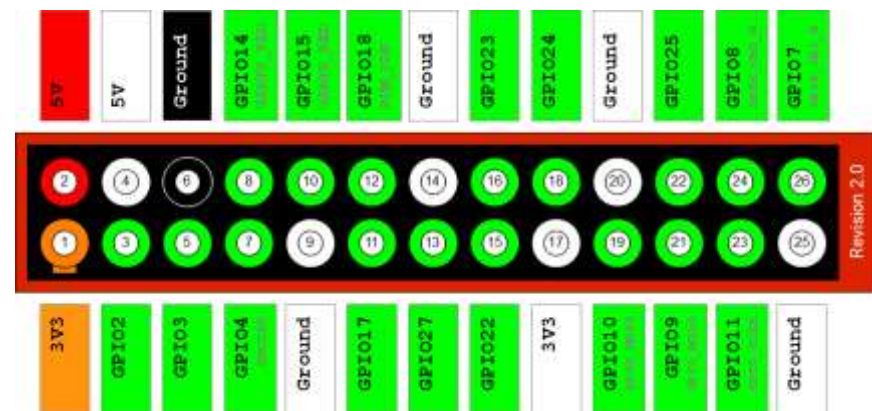The GPIO connector pin numbers are shown within the black box:



<http://www.raspberrypi-spy.co.uk/2012/09/raspberry-pi-board-revisions/>

GOOD PRACTICE...

8

1. Try to connect to pins 1, 2 & 6 for 3.3V, 5V and Ground (0V). If you use pins 4, 9, 14, 17, 20 or 25 and have problems then go back to using 1, 2 & 6.
2. Always connect the LED flat (-ve end) to ground. It makes it much easier to spot if it is the wrong way round.
3. Raspberry Pi uses 3.3V logic, so input circuits should be connected to 3V3 (pin 1) and not the 5V pin 2.

GPIOFlashcardsDLv3.doc

CONNECTOR PIN 22: FLASHING LED 10

```
# import libraries
import RPi.GPIO as GPIO
import time

# set up a pin/signal name as an output
GPIO.setmode(GPIO.BCM) # use BCM signalnames
GPIO.setup(25,GPIO.OUT)# -> connector pin 22

while True:                # loop forever
    GPIO.output(25,True)    # conn pin 22 high
    time.sleep(1.25)        # wait 1.25s
    GPIO.output(25,False)  # conn pin 22 low
    time.sleep(0.25)        # wait 0.25s
```

GPIOFlashcardsDLv3.doc

UNDERSTANDING THE GPIO PINS


9

If we want to make the LED flash using a particular GPIO connector pin, we have to understand how that pin is controlled.

1. Using flashcards 6 or 7, find pin 22 on the GPIO connector pins within the black box.
2. Each GPIO connector pin is controlled using a 'signal name'. Use the connector map to find the signal name for connector pin 22 (GPIO25).
3. ALWAYS keep the GPIO connector map to hand as the signal name is very unobvious.

GPIOFlashcardsDLv3.doc

CONNECTOR PIN 22: FLASHING LED 11

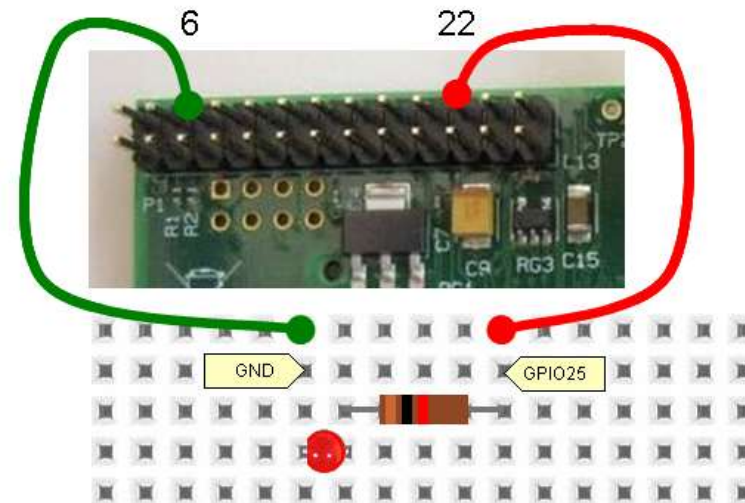

GPIOFlashcardsDLv3.doc

INPUT HI, OUTPUT HI PROGRAM

12

```
# import library
import RPi.GPIO as GPIO

# set up pin/signal name inputs & outputs
GPIO.setmode(GPIO.BCM) # use BCM signalnames
GPIO.setup(7,GPIO.OUT) # conn pin26 is output
GPIO.setup(4,GPIO.IN) # conn pin7 is input


while True:
    if GPIO.input(4)==True: # pin7:input=hi
        GPIO.output(7,True) # pin26:high

    if GPIO.input(4)==False: # pin7:input=lo
        GPIO.output(7,False) # pin26:lo
```

GPIOFlashcardsDLv3.doc

SWITCH INPUT CIRCUIT INFO

14

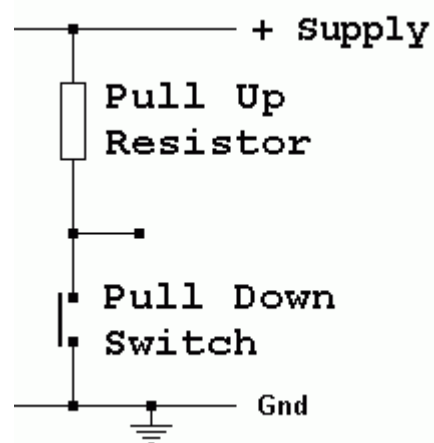

Use a 10kΩ pull-up resistor to make a 3.3V input switch. 10kΩ=BrownBlackOrange.

Attach GPIO connector pin 7 to the point between the switch and resistor.

Remember that GPIO.setup(4,GPIO.IN) sets connector pin7 as an input

GPIOFlashcardsDLv3.doc

INPUT LO, OUTPUT HI PROGRAM

13

```
# import library
import RPi.GPIO as GPIO

# set up pin/signal name inputs & outputs
GPIO.setmode(GPIO.BCM) # use BCM signalnames
GPIO.setup(7,GPIO.OUT) # conn pin26 is output
GPIO.setup(4,GPIO.IN) # conn pin7 is input


while True:
    if GPIO.input(4)==True: # pin7:input=hi
        GPIO.output(7,False) # pin26:lo

    if GPIO.input(4)==False: # pin7:input=lo
        GPIO.output(7,True) # pin26:high
```

GPIOFlashcardsDLv3.doc

SWITCH INPUT CIRCUIT (PIN 7)

15

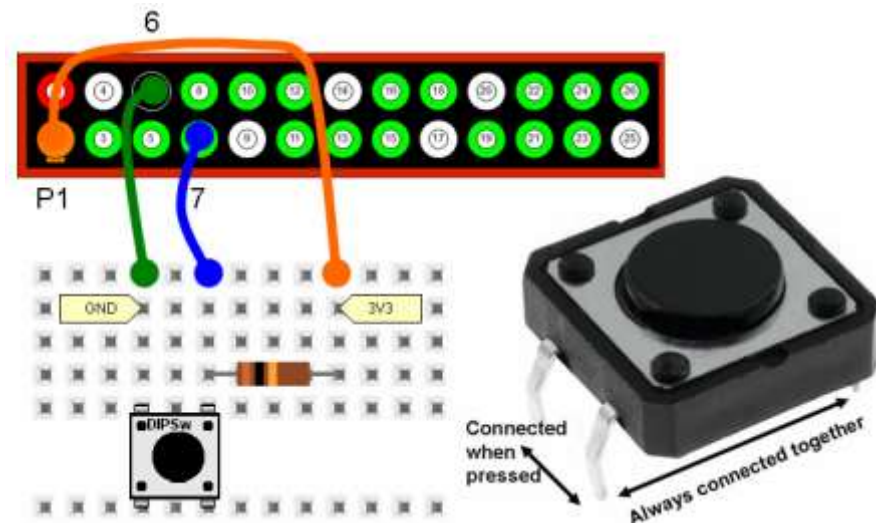

GPIOFlashcardsDLv3.doc

SERVO OUTPUT CIRCUIT INFO

16

Servos often need **external power** and a 330Ω resistor in line with the control wire



Servos rotate about a 270° degree range. To control them they need a pulse every 20ms (0.02s).

The pulse width should be 0.75ms to 2.25ms. The wider the pulse, the more it rotates.

Give the servo time to get to its position before you change it.

GPIOFlashcardsDLv3.doc

RELAY OUTPUT CIRCUIT INFO

18




A relay allows a small current flowing through the middle 2 pins to connect a switch between the outer 2 pins.

This is a great way to control circuits you have made with the Pi. The circuit you attach to the outer pins must have its own power supply to make it work.

GPIOFlashcardsDLv3.doc

SERVO OUTPUT CIRCUIT (PIN 26)

17

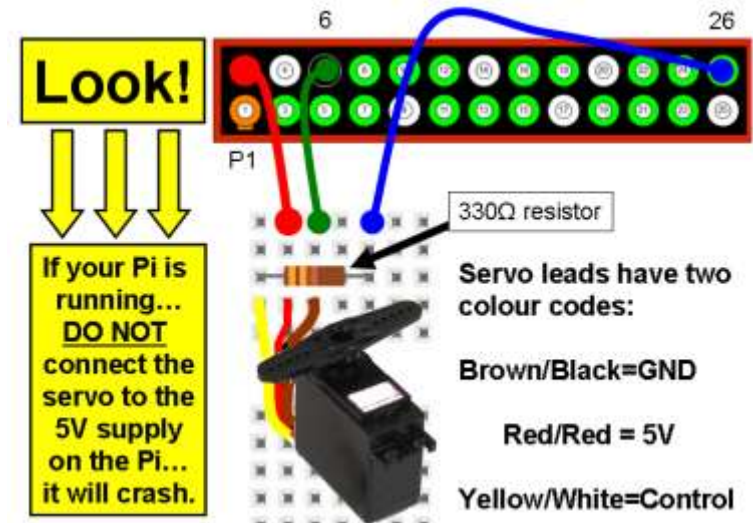


GPIOFlashcardsDLv3.doc

RELAY OUTPUT CIRCUIT (PIN 26)

19

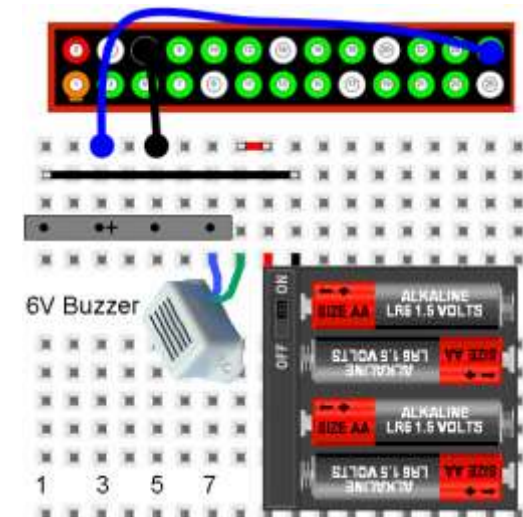
A 3.3V signal (from pin 26) is used to switch a higher voltage, higher current buzzer circuit. Top of relay → → →



GPIOFlashcardsDLv3.doc


LED OUTPUT CIRCUIT (PIN 26)

20

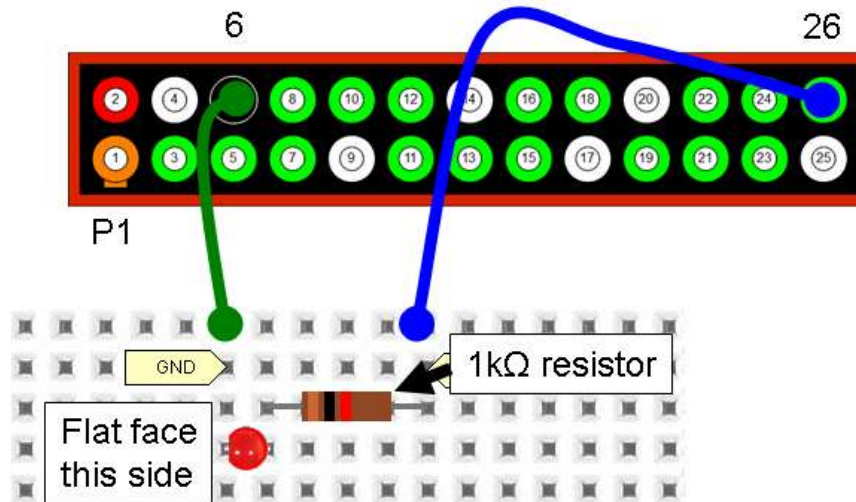

LDR INPUT CIRCUIT (PIN 7)

21

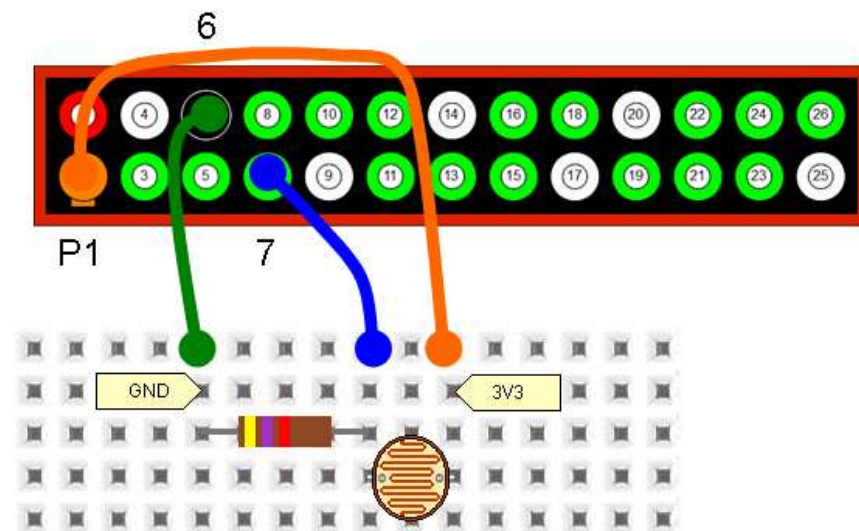


GPIOFlashcardsDLv3.doc

PIR INPUT CIRCUIT INFO

22

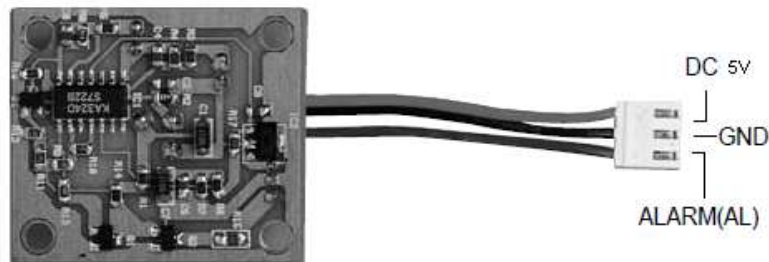The PIR unit detects infra-red light from living objects. If an object is detected it acts like a pull-down switch and connects the ALARM wire to GND. Use a 10kΩ pull-up resistor (to 3.3V) on the alarm wire.




<http://www.skpang.co.uk/catalog/pir-motion-sensor-p-796.html>

GPIOFlashcardsDLv3.doc

GPIOFlashcardsDLv3.doc

PIR INPUT CIRCUIT (PIN 7)

23

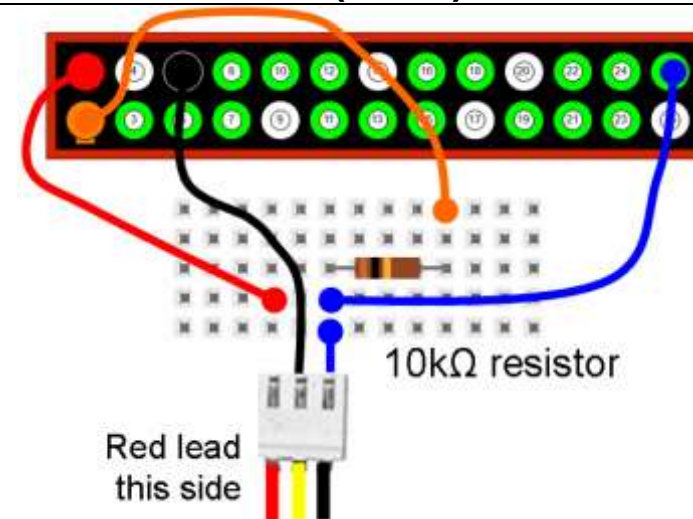

GPIOFlashcardsDLv3.doc

```

#Version 3.2: Frank Everest, David Whale, James Dalley
# December 2013

#Basic servo demo code for GPIO connector pin 26 (signal name GPIO7)
#
# >>>>>> Do NOT power-up the servo using the Pi's 5V <<<<<<<<<<
# >>>>>> if you are looking at this code! <<<<<<<<<<
#
# Shut down the Pi, take out the power lead, connect the servo
# check the wiring, recheck, then reboot the Pi, run and enjoy/adapt.

#import libraries
import RPi.GPIO as GPIO
import time

#initialise the ports
GPIO.setmode(GPIO.BCM) #Use the BCM signal names
GPIO.setup(7,GPIO.OUT) #GPIO connector pin 26 (signal name GPIO7)

#Servo parameters
# Short pulse: servo swings one way, long pulse: swings other way.
# The pulse width determines the servo's final position.
# Must repeat every 20ms
SHORTEST = 0.001 # 1ms = 0.001s
LONGEST = 0.00225 # 2.25ms = 0.00225s
PERIOD = 0.02 # 20ms = 0.02s

#Function to send one pulse to the servo
def PWM(ON, OFF):
    # (ON + OFF) must be = the repetition rate: 20ms for this demo
    GPIO.output(7,True)
    time.sleep(ON) # pulse width determines final position
    GPIO.output(7,False)
    time.sleep(OFF) # makes up the remaining 20ms

#Function to send 20 pulses to the servo
# This gives servo time to get to get into position)
# Servo will jitter if you give it too little time
def send_command(PULSE):
    #PULSE should be in the range 0.001 to 0.00225 seconds
    for pulseNumber in range(20): # can increase/decrease from 20
        PWM(PULSE,PERIOD-PULSE)

#Main code
# Makes servo swing one way, wait, then the other
# Press Ctrl+c on keyboard to stop the code and exit properly
try:
    while True:
        send_command(LONGEST) # swing one way (to a position)
        time.sleep(1) # wait one sec
        send_command(SHORTEST) # swing other way (to new position)
        time.sleep(1) # wait one sec
except:
    GPIO.cleanup() # tidy-up the GPIO ports before exiting

```